

# Transmission Gate

Vatsal B Patel, Vishwakarma Government Engineering College

June 28, 2021

## Abstract

The Transmission Gate, (TG) is a bilateral switch where either of its terminals can be the input or the output. and the third connection called the Control, which determines the switching state of the gate as an open or closed switch. The combination of an NMOS and a PMOS transistor together within a single gate means that the NMOS transistor will transfer a good logic “0” but a poor logic “1”, while the PMOS transistor transfers a good logic “1” but a poor logic “0”. Therefore, connecting an NMOS transistor with a PMOS transistor in parallel provides a single bilateral switch which offers efficient output drive capability for CMOS logic gates controlled by a single input logic level.

## 1 Circuit Details

The Transmission Gate, (TG) is a bilateral switch where either of its terminals can be the input or the output. Along with the input and output terminals, the transmission gate has a third connection called the Control, which determines the switching state of the gate as an open or closed (NO/NC) switch. The combination of an NMOS and a PMOS transistor together within a single gate means that the NMOS transistor will transfer a good logic “0” but a poor logic “1”, while the PMOS transistor transfers a good logic “1” but a poor logic “0”. Therefore, connecting an NMOS transistor with a PMOS transistor in parallel provides a single bilateral switch which offers efficient output drive capability for CMOS logic gates controlled by a single input logic level. Working of Transmission Gate When the voltage on the Control node is a logic 1, allowing both transistors to conduct and pass the signal at A to B. When the voltage on node Control is a logic 0, turning both transistors off and forcing a high-impedance condition. Thus the transmission gate acts as a “closed” switch when  $V(\text{Control}) = 1$ , while the gate acts as an “open” switch when  $V(\text{Control}) = 0$  operating as a voltage-controlled switch. Boolean Expression  $B = A \cdot \text{Control}$  We can see that the output at B relies not only on the logic level of input A but also on the logic level present on the control input. Thus the logic level value of B is defined as both A AND Control.

## 2 Implemented Circuit

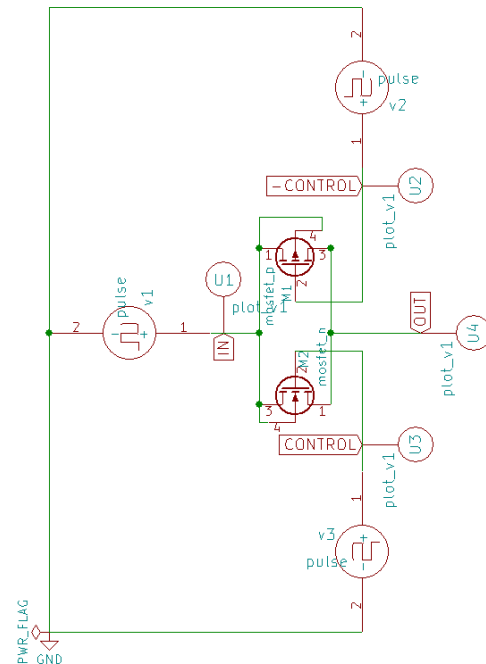


Figure 1: Reference circuit diagram.

## 3 Implemented Waveforms

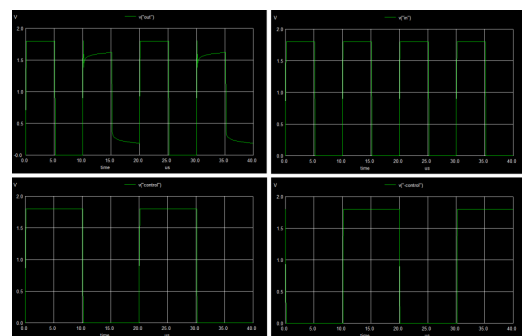


Figure 2: Reference waveform.

## References

- [1] E. Tutorials. Transmission gate as cmos bilateral switch. <https://www.electronicstutorials.ws/combination/transmission-gate.html>.